

1. What is the best way to learn how to read and interpret schematics for CS 2040 Embedded Systems?

- a. By taking a course on the subject
- b. By reading a book on the subject
- c. By studying the schematics for a particular system
- d. By asking someone who is already familiar with the subject

2. What is the most important thing to remember when reading and interpreting schematics for CS 2040 Embedded Systems?

- a. The meaning of the symbols used in the schematics
- b. The order in which the components are connected
- c. The voltage levels of the various components
- d. All of the above

3. Which of the following is NOT a type of component that is typically found in a schematic for CS 2040 Embedded Systems?

- a. Resistors
- b. Capacitors
- c. Inductors
- d. Transistors

4. What does a resistor do in a circuit?

- a. It increases the voltage of the circuit
- b. It decreases the voltage of the circuit
- c. It allows current to flow through the circuit
- d. It blocks current from flowing through the circuit

5. What does a capacitor do in a circuit?

- a. It increases the voltage of the circuit
- b. It decreases the voltage of the circuit
- c. It allows current to flow through the circuit
- d. It blocks current from flowing through the circuit

6. What does an inductor do in a circuit?

- a. It increases the voltage of the circuit
- b. It decreases the voltage of the circuit
- c. It allows current to flow through the circuit
- d. It blocks current from flowing through the circuit

7. What does a transistor do in a circuit?

- a. It increases the voltage of the circuit
- b. It decreases the voltage of the circuit
- c. It allows current to flow through the circuit
- d. It blocks current from flowing through the circuit

8. What is the purpose of a ground symbol in a schematic?

- a. To indicate that a component is connected to the ground
- b. To indicate that a component is not connected to the ground
- c. To indicate that a component is connected to a power source
- d. To indicate that a component is not connected to a power source

9. What is the purpose of a power symbol in a schematic?

- a. To indicate that a component is connected to the ground
- b. To indicate that a component is not connected to the ground
- c. To indicate that a component is connected to a power source
- d. To indicate that a component is not connected to a power source

10. Which of the following is NOT a type of connection that is typically found in a schematic?

- a. Parallel
- b. Series
- c. Ground
- d. Power

Answer Key:

- 1. d
- 2. d
- 3. c
- 4. b
- 5. c
- 6. d
- 7. c
- 8. a
- 9. c
- 10. c